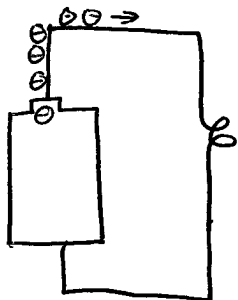


# Electron Flow



- electrons exist everywhere in the wires
- an electron attempting to leave the battery will push against an electron already in the wire, causing it to move away by electron repulsion.
- individual electrons do not flow in circles through the circuit

## Resistance


- resistor use/remove energy from the circuit.
  - the electrons do not slow down, lose their negative charge, or be destroyed, they simply lose energy
- measured in Ohms ( $\Omega$ )

## Ohm's Law

- describes the relationship between voltage ( $V$ ), current ( $I$ ), and resistance ( $R$ )

$$V = IR$$

units (V) (A)( $\Omega$ )

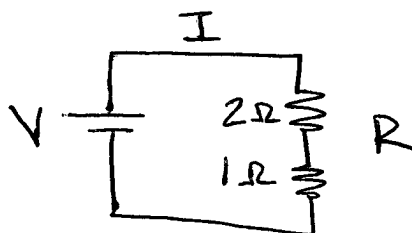

Total resistance =  $3\Omega$