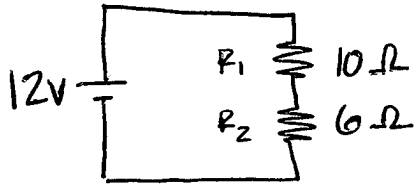


Ohm's Law in Circuits

Series



$$V_T = V_1 + V_2$$

$$R_T = R_1 + R_2$$

$$I_T = I_1 = I_2$$

Ex: $V_T = 12V$

$$R_T = 10\Omega + 6\Omega = 16\Omega$$


$$I_T = 0.75A$$

$$V_T = R_T I_T$$

$$\frac{12}{16} = \frac{16 I}{16}$$

$$0.75A = I$$

Parallel

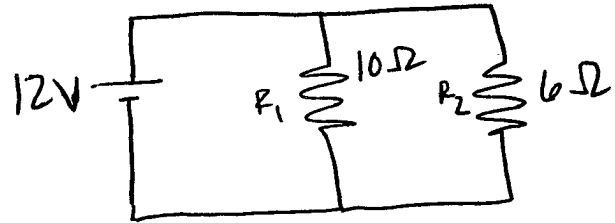

$$V_T = V_1 = V_2$$

$$I_T = I_1 + I_2$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

Ex: $V_T = 12V$

$$R_T = \frac{1}{\frac{1}{10} + \frac{1}{6}}$$

$$= \frac{1}{\frac{3}{30} + \frac{5}{30}}$$

$$= \frac{1}{\frac{8}{30}}$$

$$= \frac{30}{8}$$

$$= 3.75\Omega$$

$$I_T = I_1 + I_2$$

$$= \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$= \frac{12}{10} + \frac{12}{6} = 1.2 + 2 = 3.2A$$